

Name: SalahDin Ahmed Salh Rezk
ID: 202201079
Date: May 20, 2024



Introduction to Electronics (CIE 212)
Lab Assignment 3

1.

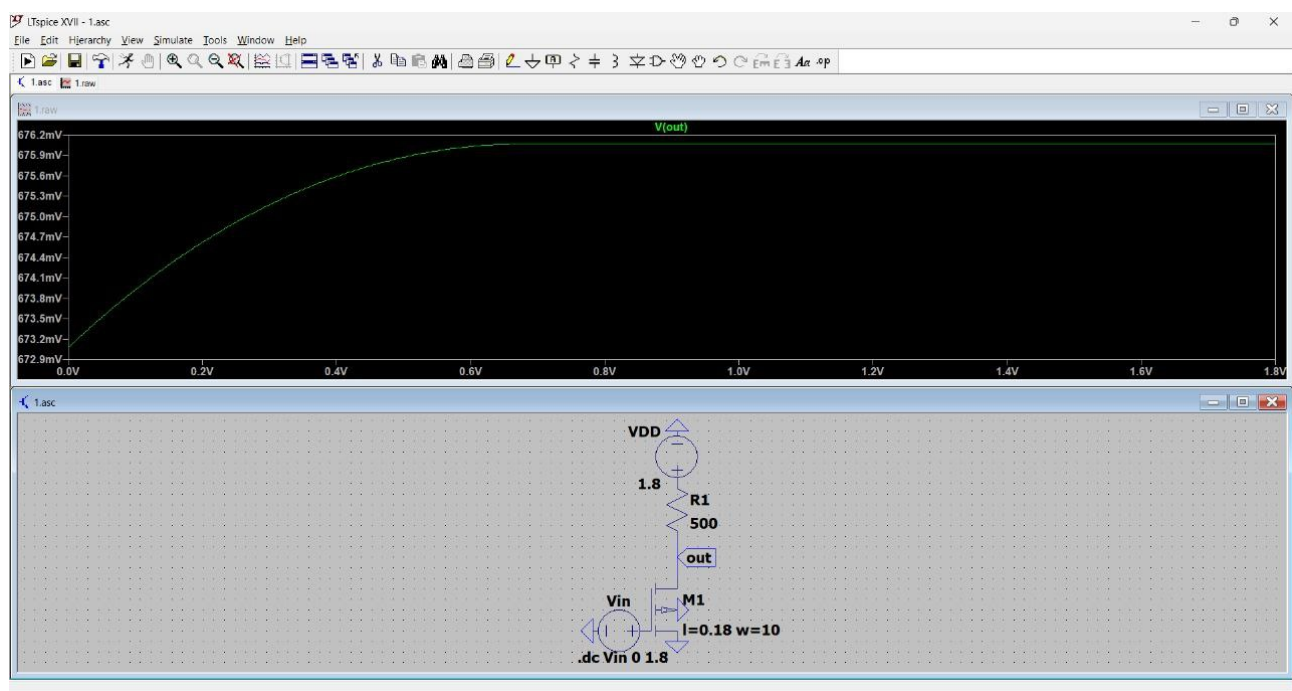


Figure 1

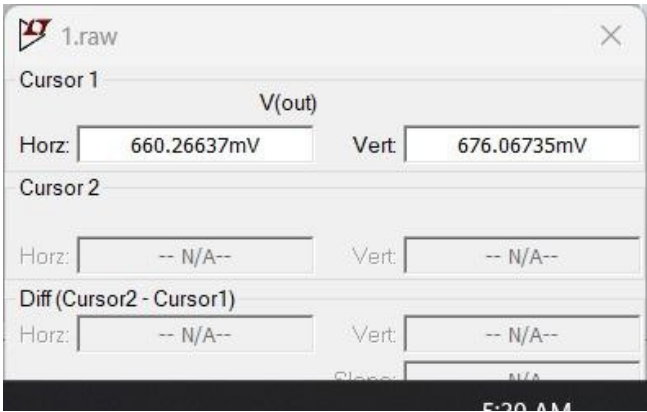


Figure 2

The cursor shows that the value at which the slope reaches maximum is 0.66V.

2.

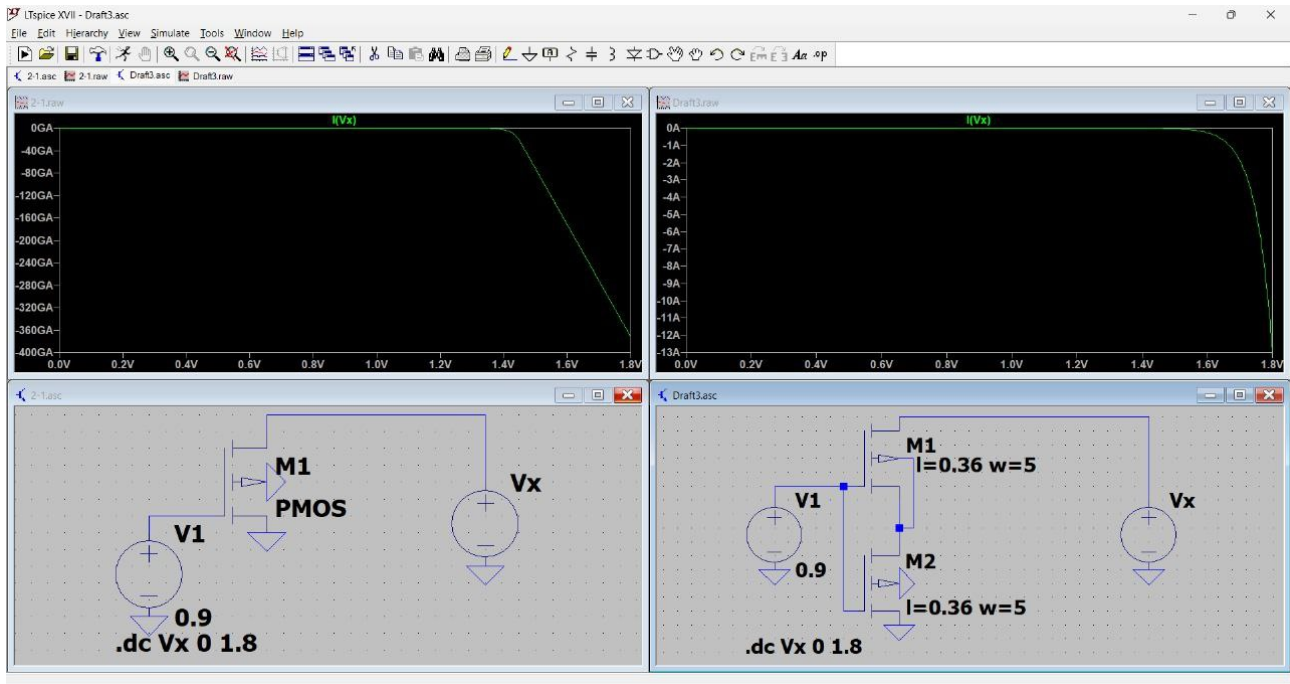


Figure 3

The two circuits are not equivalent the graph of the I_x is different for each one.