



## Electric Circuits (ENGR 210)

### Final Project

---

## Contents

<b>1</b>	<b>Problem Statements</b>	<b>2</b>
<b>2</b>	<b>Part 1</b>	<b>2</b>
2.1	Circuit 1 . . . . .	2
2.2	Circuit 2 . . . . .	3
2.3	LTspice Simulation . . . . .	4
<b>3</b>	<b>Part 2</b>	<b>5</b>
3.1	Cascading the two circuits . . . . .	5
3.2	LTspice Simulation . . . . .	6

## List of Figures

1	Non-inverting amplifier . . . . .	3
2	Voltage divider . . . . .	4
3	LTspice simulation results of the two circuits . . . . .	4
4	LTspice simulation results of the cascaded circuits . . . . .	6

## List of Tables

1	Circuit 1 and Circuit 2 parameters . . . . .	2
2	LTspice simulation results . . . . .	5
3	LTspice simulation results . . . . .	7

## Listings

1	LTspice simulation results of the two circuits . . . . .	4
2	LTspice simulation results of the cascaded circuits . . . . .	6

### Abstract

This report describes the design of two circuits, Circuit 1 and Circuit 2, that meet the requirements specified in the project description. The theoretical values of the output voltages of the two circuits are calculated and compared to the simulation results. The two circuits are then cascaded, and the theoretical value of the output voltage of the cascaded circuits is calculated and compared to the simulation results. The simulation show that the theoretical values are very close to the simulation results.

# 1 Problem Statements

Design two circuits, Circuit 1 and Circuit 2, that meet the following requirements:

1. Circuit 1 should have an output voltage,  $V_{o1}$ , equal to  $K_a$  times the input voltage,  $V_{i1}$ .
2. Circuit 2 should have an output voltage,  $V_{o2}$ , equal to  $K_b$  times the input voltage,  $V_{i2}$ .
3. The values of  $K_a$  and  $K_b$  can be found in a provided resource, and each circuit should use a different value for  $K_a$  and  $K_b$ .
4. The circuits should adhere to the following design constraints:
  - (a) Resistors with resistance values ranging from  $1\text{K}\Omega$  to  $10\text{K}\Omega$  can be used.
  - (b) If an op-amp is used, only one op-amp is allowed.
  - (c) The circuits should be designed using the fewest components possible.
5. Use the two circuits you have designed in part 1, cascade them.  
Is the equation  $V_{o2} = K_a \cdot K_b \cdot V_{i1}$  satisfied?
  - (a) Verify your answer using LTspice.
  - (b) Explain why the answer is 'YES' or 'NO'.
  - (c) If your answer is 'NO', redesign the circuit to meet the requirements in part 1 and satisfy the equation  $V_{o2} = K_a \cdot K_b \cdot V_{i1}$ .

## 2 Part 1

Table 1: Circuit 1 and Circuit 2 parameters

$K_a$	$K_b$	$V_{i1}$	$V_{i2}$
2.4	0.65	1V	1V

Based on the requirements in Section 1 and the provided parameters in Table 1, the first circuit needs to have an output voltage,  $V_{o1}$ , equal to 2.4 times the input voltage,  $V_{i1}$ , and the second circuit needs to have an output voltage,  $V_{o2}$ , equal to 0.65 times the input voltage,  $V_{i2}$ . This means that the first circuit needs to be an amplifier with a gain of 2.4, and the second circuit needs to be an attenuator with a gain of 0.65.

### 2.1 Circuit 1

As mentioned, the first circuit needs to be an amplifier with a gain of 2.4. To achieve this, an operational amplifier (op-amp) is used. The op-amp is configured in a non-inverting amplifier configuration. The gain of the non-inverting amplifier is given by Equation 1.

$$K_a = A_v = 1 + \frac{R_2}{R_1} \quad (1)$$

The gain of the non-inverting amplifier is equal to the ratio of the feedback resistor,  $R_2$ , and the input resistor,  $R_1$ , plus one. The feedback resistor is connected between the output of

the op-amp and the inverting input of the op-amp. The input resistor is connected between the inverting input of the op-amp and the input voltage,  $V_{i1}$ . The output voltage,  $V_{o1}$ , is connected between the output of the op-amp and the inverting input of the op-amp.

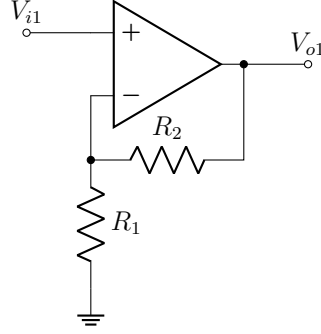


Figure 1: Non-inverting amplifier

Since the input voltage,  $V_{i1}$ , is 1V, the output voltage,  $V_{o1}$ , needs to be 2.4V. The feedback resistor is chosen to be  $1K\Omega$ , and the input resistor is chosen to be  $1.4K\Omega$ . The gain of the non-inverting amplifier is then shown in Equation 2

$$1 + \frac{1.4K\Omega}{1K\Omega} = 2.4 \quad (2)$$

However, the op-amp needs to be supplied with voltage. VCC is connected to the positive supply voltage, and -VCC is connected to the negative supply voltage. VCC is equal to 5V, and -VCC is equal to -5V. As the input voltage,  $V_{i1}$ , is 1V, the output voltage,  $V_{o1}$ , will be 2.4V so 5V is enough to supply the op-amp.

## 2.2 Circuit 2

As mentioned, the second circuit needs to be an attenuator with a gain of 0.65. To achieve this, a voltage divider is used. The voltage divider is made up of two resistors,  $R_1$  and  $R_2$ . The output voltage,  $V_{o2}$ , is connected between the two resistors, and the input voltage,  $V_{i2}$ , is connected to one of the resistors. The output of the voltage divider is given by Equation 3.

$$V_{o2} = V_{i2} \cdot \frac{R_2}{R_1 + R_2} \quad (3)$$

It is possible, then, to rewrite the equation to solve for  $R_2$  as shown in Equation 4. The input voltage,  $V_{i2}$ , is 1V, and the output voltage,  $V_{o2}$ , needs to be 0.65V. The value of  $R_1$  is chosen to be  $1K\Omega$ , and the value of  $R_2$  is then calculated to be  $1.857K\Omega$ .

$$R_2 = \frac{V_{o2} \cdot R_1}{V_{i2} - V_{o2}} = \frac{0.65 \cdot 1K\Omega}{1V - 0.65V} = 1.857K\Omega \quad (4)$$


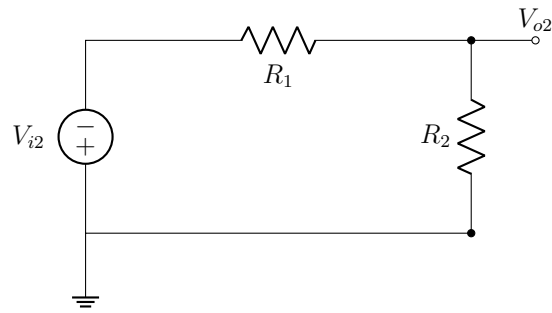


Figure 2: Voltage divider
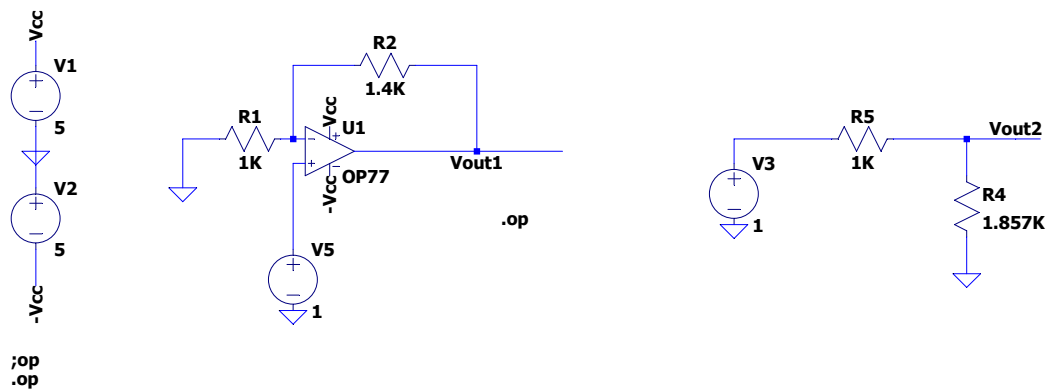
## 2.3 LTspice Simulation

The two circuits are simulated using LTspice. The simulation circuit is shown in Figure 3. The simulation results are shown in Listing 1.



--- C:\Users\salah\AppData\Local\Microsoft\Windows\NetCache\IE\2MAK2A1Q\circuits1&2[1].asc ---

Figure 3: LTspice simulation results of the two circuits

```

1      --- Operating Point ---
2
3 V(n001):      1.00001      voltage
4 V(n003):      1      voltage
5 V(vcc):      5      voltage
6 V(-vcc):      -5      voltage
7 V(vout1):      2.40003      voltage
8 V(vout2):      0.649983      voltage
9 V(n002):      1      voltage
10 I(R5):      -0.000350018      device_current
11 I(R4):      0.000350018      device_current

```

```

12 I(R2): 0.00100001 device_current
13 I(R1): 0.00100001 device_current
14 I(V3): -0.000350018 device_current
15 I(V5): -1.34601e-009 device_current
16 I(V2): -0.00075 device_current
17 I(V1): -0.00175001 device_current
18 Ix(u1:1): 1.34601e-009 subckt_current
19 Ix(u1:2): 1.046e-009 subckt_current
20 Ix(u1:99): 0.00175001 subckt_current
21 Ix(u1:50): -0.00075 subckt_current
22 Ix(u1:39): -0.00100001 subckt_current

```

Listing 1: LTspice simulation results of the two circuits

From the simulation results, it can be seen that the output voltage,  $V_{o1}$ , is 2.40003V and the output voltage,  $V_{o2}$ , is 0.649983V. These values are very close to the theoretical values of 2.4V and 0.65V, respectively. Table 2 shows the simulation results.

Table 2: LTspice simulation results

$V_{i1}$	1V
$V_{i2}$	1V
$V_{o1}$	2.40003V
$V_{o2}$	0.649983V

## 3 Part 2

### 3.1 Cascading the two circuits

The output voltage,  $V_{o1}$ , is connected to the input voltage,  $V_{i2}$ , of the second circuit. The output voltage,  $V_{o2}$ , is then measured. The expected result is that the output voltage,  $V_{o2}$ , is equal to  $K_a \cdot K_b \cdot V_{i1}$ , which is equal to 1.56V, as shown below.

$$V_{i1} = 1V \quad (5)$$

$$V_{i2} = V_{o1} = K_a \cdot V_{i1} \quad (6)$$


$$= 2.4 \cdot 1V = 2.4V \quad (7)$$

$$V_{o2} = V_{i2} \cdot \frac{R_2}{R_1 + R_2} \quad (8)$$

$$= 2.4V \cdot \frac{1.857K\Omega}{1K\Omega + 1.857K\Omega} \quad (9)$$

$$= 1.56V. \quad (10)$$

## 3.2 LTspice Simulation

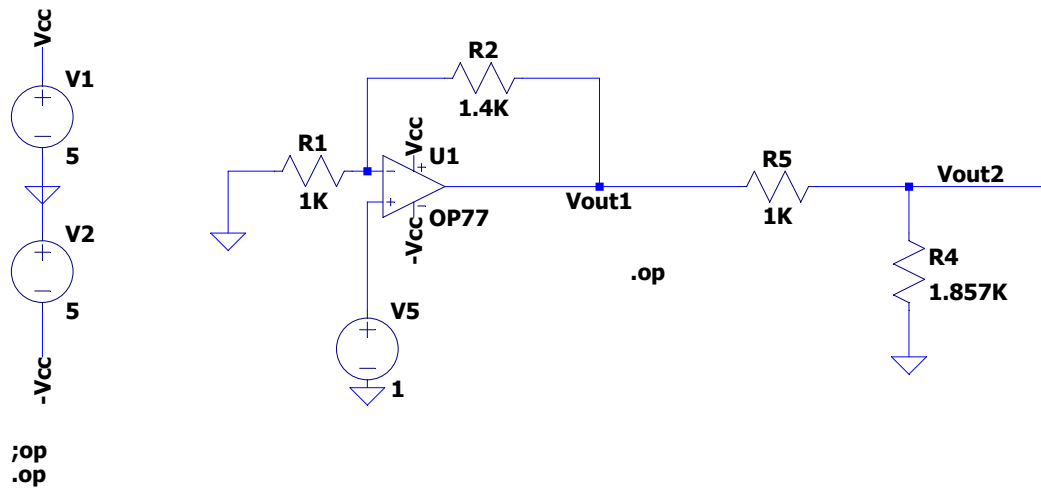

--- C:\Users\salah\AppData\Local\Microsoft\Windows\NetCache\IE\2MAK2A1Q\circuits1&2[1].asc ---

Figure 4: LTspice simulation results of the cascaded circuits

```

1      --- Operating Point ---
2
3 V(n001):      1.00001      voltage
4 V(n003):      1      voltage
5 V(vcc):      5      voltage
6 V(-vcc):      -5      voltage
7 V(vout):      2.40003      voltage
8 V(n002):      1.55997      voltage
9 I(R5):      -0.000840051      device_current
10 I(R4):      0.000840051      device_current
11 I(R2):      0.00100001      device_current
12 I(R1):      0.00100001      device_current
13 I(V5):      -1.34601e-009      device_current
14 I(V2):      -0.00075      device_current
15 I(V1):      -0.00259006      device_current
16 Ix(u1:1):      1.34601e-009      subckt_current
17 Ix(u1:2):      1.046e-009      subckt_current
18 Ix(u1:99):      0.00259006      subckt_current
19 Ix(u1:50):      -0.00075      subckt_current
20 Ix(u1:39):      -0.00184006      subckt_current

```

Listing 2: LTspice simulation results of the cascaded circuits

From the simulation results, it can be seen that the output voltage,  $V_{o1}$ , is 2.40003V and the output voltage,  $V_{o2}$ , is 1.55997V. These values are very close to the theoretical values of 2.4V and 1.56V, respectively. Table 3 shows the simulation results. From these results, it can be seen that the equation  $V_{o2} = K_a \cdot K_b \cdot V_{i1}$  is satisfied.

Table 3: LTspice simulation results

$V_{i1}$	1V
$V_{o1}$	2.40003V
$V_{o2}$	1.55997V

$$V_{o2} = K_a \cdot K_b \cdot V_{i1} = 2.4 \cdot 0.65 \cdot 1V = 1.56V \quad (11)$$