

Student Name: SalahDin Rezk
Student ID: 202201079
Date: November 4, 2023



Electric Circuits (ENGR210)

Assignment 2

1. If the interconnection in Figure 1 is valid, find the total power developed in the circuit. If the interconnection is not valid, explain why.

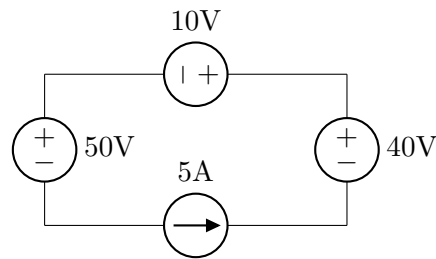


Figure 1

KVL on loop:

$$-50 - 10 + 40 + V_{\text{source}} = 0 \quad (1)$$

$$V_{\text{source}} = 20 \text{ V}. \quad (2)$$

$$40 \times -5 = -200 \text{ W} \quad (3)$$

$$10 \times 5 = 50 \text{ W} \quad (4)$$

$$50 \times 5 = 250 \text{ W} \quad (5)$$

$$-20 \times 5 = -100 \text{ W} \quad (6)$$

$$\Sigma P = -200 + 50 + 250 - 100 \quad (7)$$

$$= 0. \quad (8)$$

2. The interconnection of ideal sources can lead to an indeterminate solution. With this thought in mind, explain why the solutions for v_1 and v_2 in the circuit in Figure 2 are not unique.

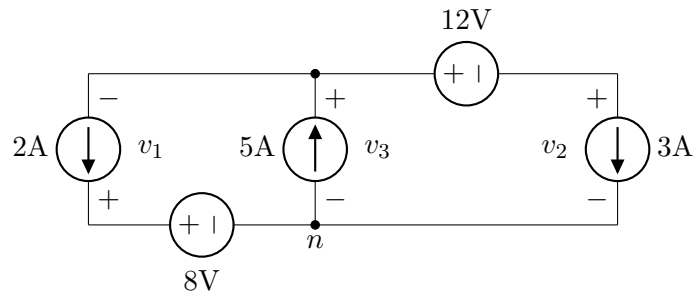


Figure 2

KCL at node n :

$$\Sigma I = 0 \quad (9)$$

$$3 + 2 - 5 = 0 \implies \text{System is valid.} \quad (10)$$

KVL on loop:

$$12 - v_3 + v_2 = 0 \quad (11)$$

$$v_1 - 8 + v_3 = 0. \quad (12)$$

From (11) and (12) the system of equations is free and there is no unique solution.

3. The current i_x the circuit shown in Figure 3 is 50 mA and the voltage v_x is 3.5 V. Find

$$i_x = 50 \text{ mA} \quad v_x = 3.5 \text{ V.} \quad (13)$$

(a) i_1 .

$$i_1 = \frac{v_x}{R} \quad (14)$$

$$= \frac{3.5}{175} \quad (15)$$

$$= 20 \text{ mA.} \quad (16)$$

(b) v_1 .

Applying KCL:

$$i_x = i_1 + i_2 \quad (17)$$

$$50 = 20 + i_2 \quad (18)$$

$$i_2 = 30 \text{ mA.} \quad (19)$$

$$v_1 = i_2 \times R \quad (20)$$

$$= 30 \times 10^{-3} \times 250 \quad (21)$$

$$= 7.5 \text{ V.} \quad (22)$$

(c) v_g .

Using KVL:

$$v_1 + 50i_x - v_g = 0. \quad (23)$$

$$v_g = v_1 + 50i_x \quad (24)$$

$$= 7.5 + 50 \times 50 \times 10^{-3} \quad (25)$$

$$= 10 \text{ V.} \quad (26)$$

(d) the power supplied by the voltage source.

$$P = v_g i_x = 10 \times 50 \times 10^{-3} \quad (27)$$

$$= 0.5 \text{ W.} \quad (28)$$

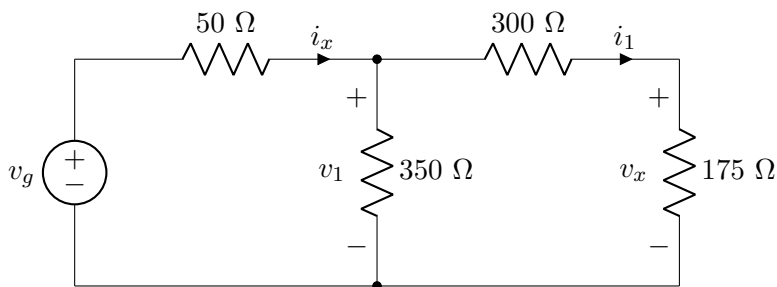


Figure 3