

Student Name: SalahDin Rezk
 Student ID: 202201079
 Date: November 9, 2023



Digital Design and Computer Architecture (CIE 239)

Assignment 2

1. a. Write a Boolean equation in sum-of-products canonical form and product-of-sum canonical form for following truth table.

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>Y</i>
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

Table 1

Solution.

$$Y = A'B'C'D' + A'B'C'D + A'B'CD' + A'B'CD + AB'C'D' + AB'CD' + ABCD' \quad (1)$$

$$= \Sigma(0, 1, 2, 3, 8, 10, 14). \quad (2)$$

$$Y = (A + B' + C + D)(A + B' + C + D')(A + B' + C + D')(A + B' + C' + D) \\ (A + B' + C' + D')(A' + B + C + D')(A' + B + C' + D')(A' + B' + C + D) \\ (A' + B' + C + D')(A' + B' + C' + D') \quad (3)$$

$$= \Pi(4, 5, 6, 7, 9, 11, 12, 13, 15). \quad (4)$$

■

- b. Minimize each of the Boolean equations of the sum-of products (use Boolean algebra) and implement the simplified equation using basic logic gates (AND, OR and NOT gate).

Solution.

$$Y = A'B'C'D' + A'B'C'D + A'B'CD' + A'B'CD + AB'C'D' + AB'CD' + ABCD' \quad (5)$$

$$= A'B'C'(D' + D) + A'B'CD' + A'B'CD + AB'D'(C' + C) + ABCD' \quad (6)$$

$$= A'B'C' + A'B'CD' + A'B'CD + AB'D' + ABCD' \quad (7)$$

$$= A'B'(C' + CD') + A'B'CD + AB'D' + ABCD' \quad (8)$$

$$= A'B'(C' + D') + A'B'CD + AB'D' + ABCD' \quad (9)$$

$$= A'B'(C' + D' + CD) + AB'D' + ABCD' \quad (10)$$

$$= A'B'(C' + CD + D') + AB'D' + ABCD' \quad (11)$$

$$= A'B'(C' + D + D') + AB'D' + ABCD' \quad (12)$$

$$= A'B'(C' + 1) + AB'D' + ABCD' \quad (13)$$

$$= A'B' + AB'D' + ABCD' \quad (14)$$

$$= B'(A' + AD') + ABCD' \quad (15)$$

$$= B'(A' + D') + ABCD' \quad (16)$$

$$= A'B' + B'D' + ABCD' \quad (17)$$

$$= A'B' + D'(B' + ABC) \quad (18)$$

$$= A'B' + D'(B' + BAC) \quad (19)$$

$$= A'B' + D'(B' + AC) \quad (20)$$

$$= A'B' + B'D' + ACD'. \quad (21)$$

■

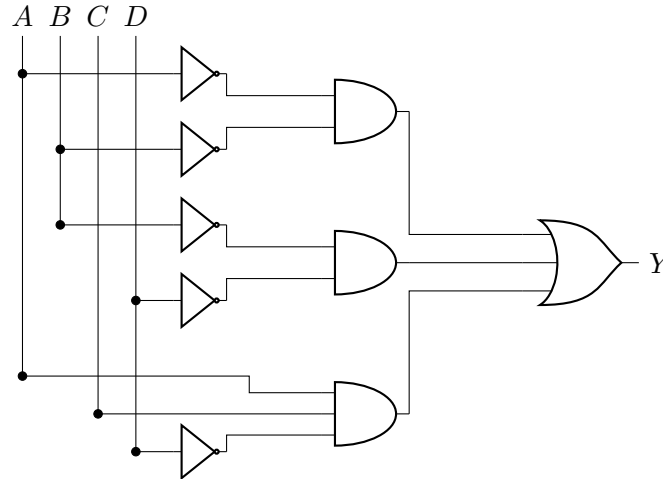


Figure 1

- c. Implement the minimized function again using only using only NOT gates and NAND and NOR gates.

Solution.

$$Y = \overline{\overline{A'B' + B'D' + ACD'}} \quad (22)$$

$$= \overline{A'B' \cdot B'D' \cdot ACD'}. \quad (23)$$

■

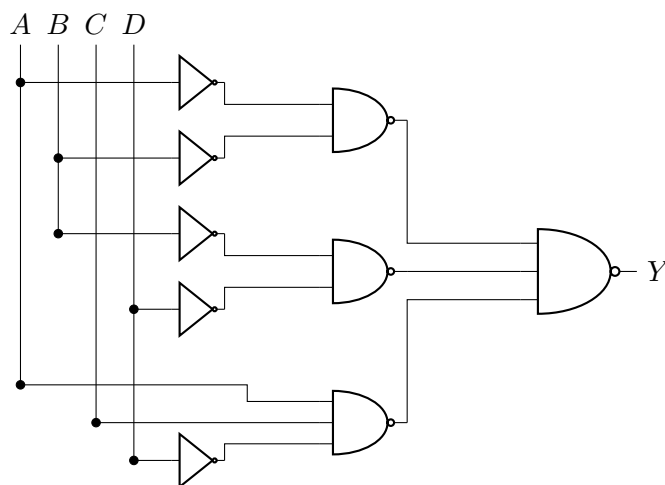


Figure 2

2. Simplify the following Boolean equations using Boolean theorems. Check for correctness using K-map.

a. $F(x, y, z) = x'y' + xyz + x'y$

Solution.

$$F(x, y, z) = x'y' + xyz + x'y \quad (24)$$

$$= x'(y' + y) + xyz \quad (25)$$

$$= x' + xyz \quad (26)$$

$$= x' + yz. \quad (27)$$

■

$\begin{matrix} z \\ x \end{matrix}$	00	01	11	10
0	1	1	1	1
1	0	0	1	0

K-Map 1

b. $F(w, x, y, z) = w'x(z' + yz) + x(w + w'yz)$

Solution.

$$F(w, x, y, z) = w'x(z' + yz) + x(w + w'yz) \quad (28)$$

$$= w'x(z' + zy) + x(w + w'yz) \quad (29)$$

$$= w'x(z' + y) + x(w + yz) \quad (30)$$

$$= w'xz' + w'xy + xw + xyz \quad (31)$$

$$= x(w + w'z') + w'xy + xyz \quad (32)$$

$$= x(w + z') + w'xy + xyz \quad (33)$$

$$= xw + xz' + w'xy + xyz \quad (34)$$

$$= xz' + x(w + w'y) + xyz \quad (35)$$

$$= xz' + x(w + y) + xyz \quad (36)$$

$$= xz' + xw + xy + xyz \quad (37)$$

$$= xz' + xw + xy(1 + z) \quad (38)$$

$$= xz' + xw + xy. \quad (39)$$

■

$\begin{smallmatrix} yz \\ wx \end{smallmatrix}$	00	01	11	10
00	0	0	0	0
01	1	0	1	1
11	1	1	1	1
10	0	0	0	0

K-Map 2

3. Simplify the following using Kmap and implement using logic gates

(a) $F(x, y, z) = \Sigma m(0, 2, 6, 7)$

$\begin{array}{c} z \\ \backslash x \end{array}$	00	01	11	10
0	1	0	0	1
1	0	0	1	1

K-Map 3

Solution.

$$F(x, y, z) = x'z' + xy. \quad (40)$$

■

(b) $F(A, B, C, D) = \Sigma m(1, 3, 6, 7, 9, 11, 12, 13)$

$\begin{array}{c} CD \\ \backslash AB \end{array}$	00	01	11	10
00	0	1	1	0
01	0	0	1	1
11	1	1	0	0
10	0	1	1	0

K-Map 4

Solution.

$$F(A, B, C, D) = ABC' + A'BC + B'D. \quad (41)$$

■

4. Using De Morgan equivalent gates and bubble pushing methods, redraw the circuit so that you can find the Boolean equation by inspection. Write the Boolean equation.

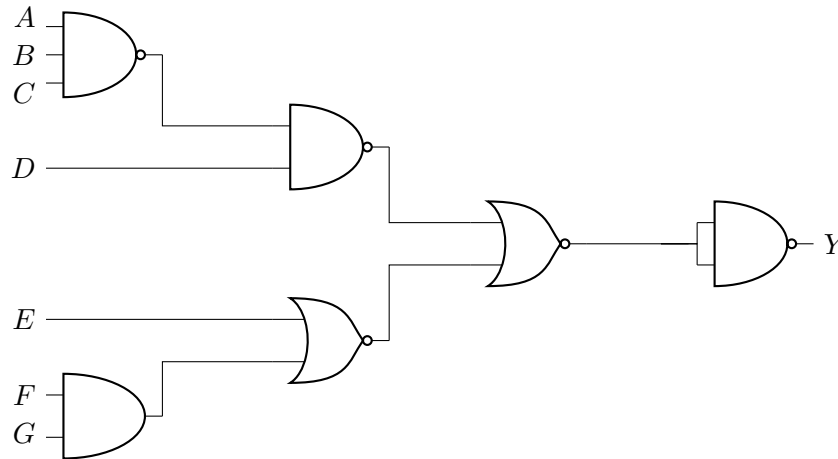


Figure 3

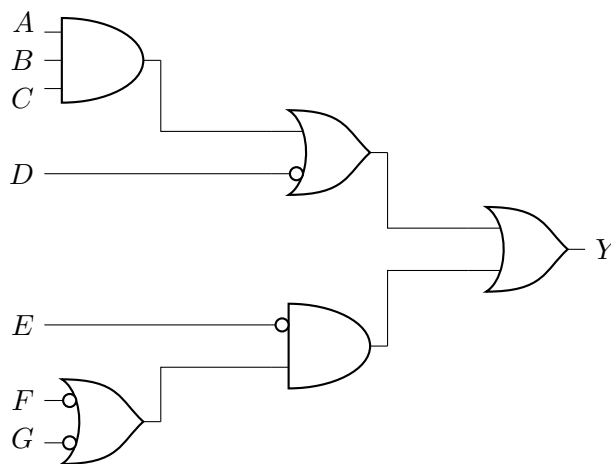


Figure 4

Solution.

$$Y = ABC + D' + E'(F' + G') \quad (42)$$

$$= ABC + D' + E'F' + E'G'. \quad (43)$$

■

5. Find a minimal Boolean equation for the function. Remember to take advantage of the don't care entries. (use k-map)

A	B	C	D	Y
0	0	0	0	X
0	0	0	1	X
0	0	1	0	X
0	0	1	1	0
0	1	0	0	0
0	1	0	1	X
0	1	1	0	0
0	1	1	1	X
1	0	0	0	1
1	0	0	1	0
1	0	1	0	X
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	X
1	1	1	1	1

Table 2

$\begin{array}{c} CD \\ AB \end{array}$	00	01	11	10
00	X	X	0	X
01	0	X	X	0
11	1	1	1	X
10	1	0	X	1

K-Map 5

Solution.

$$F(A, B, C, D) = AD + AB + B'D'. \quad (44)$$

■

6. A circuit has four inputs and two outputs. The inputs, $A_{3:0}$, represent a number from 0 to 15. Output P should be TRUE if the number is prime (0 and 1 are not prime, but 2, 3, 5, and so on, are prime). Output D should be TRUE if the number is an even number. Give simplified Boolean equations for each output and sketch a circuit (use k-map)

Dec	A_3	A_2	A_1	A_0	P	D
0	0	0	0	0	0	1
1	0	0	0	1	0	0
2	0	0	1	0	1	1
3	0	0	1	1	1	0
4	0	1	0	0	0	1
5	0	1	0	1	1	0
6	0	1	1	0	0	1
7	0	1	1	1	1	0
8	1	0	0	0	0	1
9	1	0	0	1	0	0
10	1	0	1	0	0	1
11	1	0	1	1	1	0
12	1	1	0	0	0	1
13	1	1	0	1	1	0
14	1	1	1	0	0	1
15	1	1	1	1	0	0

Table 3

A_1A_0 A_3A_2	00	01	11	10
00	0	0	1	1
01	0	1	1	0
11	0	1	0	0
10	0	0	1	0

(a) P

A_1A_0 A_3A_2	00	01	11	10
00	1	0	0	1
01	1	0	0	1
11	1	0	0	1
10	1	0	0	1

(b) D

K-Map 6

Solution.

$$D(A_3, A_2, A_1, A_0) = A'_0. \quad (45)$$

$$P(A_3, A_2, A_1, A_0) = A'_3A'_2A_1 + A'_3A_2A_0 + A_2A'_1A_0 + A'_2A_1A_0. \quad (46)$$

■

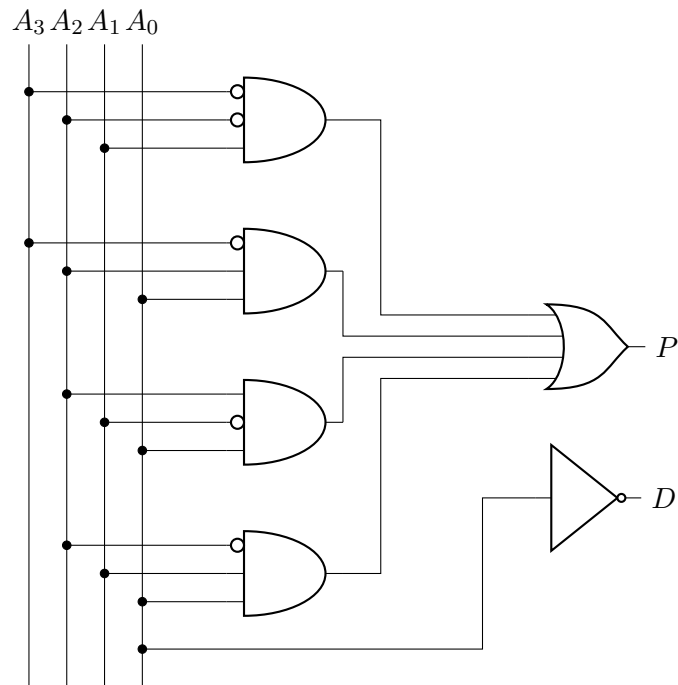


Figure 5

7. Write the HDL code for question number 6 (Your answer should include the HDL code and the input and output signal screenshot from modelsim)

SystemVerilog

```

1 module prime_even(
2     input logic [3:0] A,
3     output logic P, D
4 );
5
6     assign P = ~A[3] & ~A[2] & A[1] | ~A[3] & A[2] & A[0] | A[2] & ~A[1] & A[0]
7         | ~A[2] & A[1] & A[0];
8     assign D = ~A[0];
9 endmodule

```

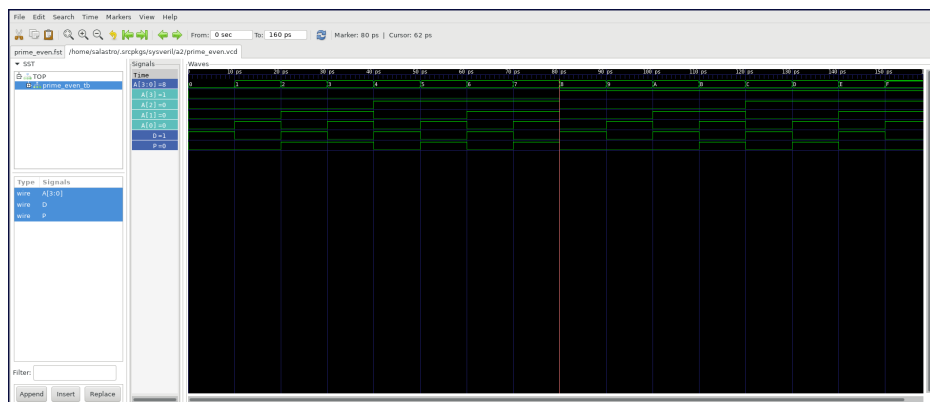


Figure 6: Waveform of prime_even using GTKWave