

## Digital Design and Computer Architecture (CIE 239)

### Assignment 4

1. Assume that registers  $R_1$  and  $R_2$  in the Figure hold two unsigned numbers. When select input  $X$  is equal to 1, the adder-subtractor circuit performs the arithmetic operation " $R_1 + 2$ 's complement of  $R_2$ ." This sum and the output carry  $C_n$  are transferred into  $R_1$  and  $C$  when  $K_1 = 1$  and a positive edge occurs on the clock.

*Solution.*

- Assume  $C = 1$ .

Perform  $R_1 - R_2$  and  $X = 1$

$\therefore R_1 = 1111$ , suppose  $R_2 = 1010$  2's complement of  $R_2$  is 0110

$R_1 - R_2 = 10101$

$\therefore R_1 = 0101$  and  $C = 1$

So if $C = 1$ then the value transferred to $R_1$ is equal to $R_2 - R_1$
---

- Assume  $C = 0$ . Perform  $R_2 - R_1$

2's complement of  $R_1$  is 1010

$R_2 - R_1 = 1101$

2's complement of  $R_2 - R_1$  is 0011

So if $C = 0$ then the 2's complement of $R_2 - R_1$ is equal to $R_1$
--

■

2. The outputs of registers  $R_0$ ,  $R_1$ ,  $R_2$ , and  $R_3$  are connected through 4-to-1 multiplexers to the inputs of a fifth register,  $R_4$ . Each register is 8 bits long. The required transfers, as dictated by four control variables, are

$$C_0 : R_4 \leftarrow R_0,$$

$$C_1 : R_4 \leftarrow R_1,$$

$$C_2 : R_4 \leftarrow R_2,$$

$$C_3 : R_4 \leftarrow R_3.$$

The control variables are mutually exclusive (i.e., only one variable can be equal to 1 at any time) while the other three are equal to 0. Also, no transfer into  $R_4$  is to occur for all control variables equal to 0.

- (a) Using registers and a multiplexer, draw a detailed logic diagram of the hardware that implements a single bit of these register transfers.

*Solution.*

 


Figure 1

- (b) Write HDL code for the design.

*Solution.*

```

1 module Q_2 (clk, reset, C[0:3], R[0:4]);
2   input clk, reset;
3   input [3:0] C;
4   input [7:0] R[0:3];
5   output [7:0] R[4];
6   reg [7:0] R[0:4];
7   always @(posedge clk, posedge reset)
8     if (reset)
9       R[0:4] <= 0;
10    else
11      case (C)
12        4'b0001: R[4] <= R[0];
13        4'b0010: R[4] <= R[1];
14        4'b0100: R[4] <= R[2];
15        4'b1000: R[4] <= R[3];
16        default: R[4] <= 0;
17      endcase
18 endmodule

```

3. You are designing an FSM to keep track of the mood of four students working in the digital design lab. Each student's mood is either HAPPY (the circuit works), SAD (the circuit

blew up), BUSY (working on the circuit), CLUELESS (confused about the circuit), or ASLEEP (face down on the circuit board). How many states does the FSM have? What is the minimum number of bits necessary to represent these states?

*Solution.*

- The FSM has  $5^4 = 625$  states.
- The minimum number of bits necessary to represent these states is  $\lceil \log_2 625 \rceil = \lceil 9.28 \rceil = 10$  bits.

■

4. You have been enlisted to design a soda machine dispenser for your department lounge. Sodas are partially subsidized by the student chapter of the IEEE, so they cost only 25 cents. The machine accepts nickels, dimes, and quarters. When enough coins have been inserted, it dispenses the soda and returns any necessary change. Design an FSM controller for the soda machine. The FSM inputs are Nickel, Dime, and Quarter, indicating which coin was inserted. Assume that exactly one coin is inserted on each cycle. The outputs are Dispense, ReturnNickel, ReturnDime, and ReturnTwoDimes. When the FSM reaches 25 cents, it asserts Dispense and the necessary Return outputs required to deliver the appropriate change. Then it should be ready to start accepting coins for another soda.

*Solution.*

■

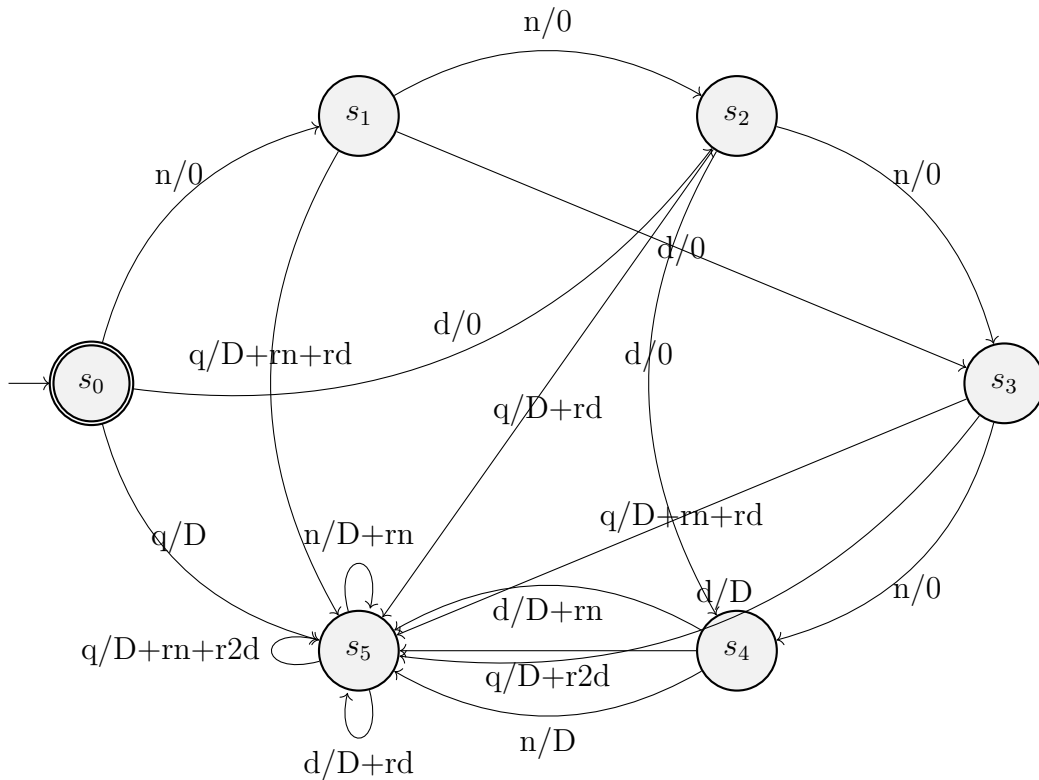


Figure 2

5. Analyze the FSM shown in the figure. Write the state transition and output tables and sketch the state transition diagram. Describe in words what the FSM does. Recall that the s and r register inputs indicate set and reset, respectively.

*Solution.*

$$D_0 = \overline{A}, \quad D_1 = Q_0A, \quad D_2 = (Q_1 + Q_2)A, \quad Q = Q_2 \quad (1)$$



$Q_0$	$Q_1$	$Q_2$	$A$	$Q'_0$	$Q'_1$	$Q'_2$	$D_0$	$D_1$	$D_2$	$Q$
0	0	0	0	0	0	0	0	0	0	0

Table 1