
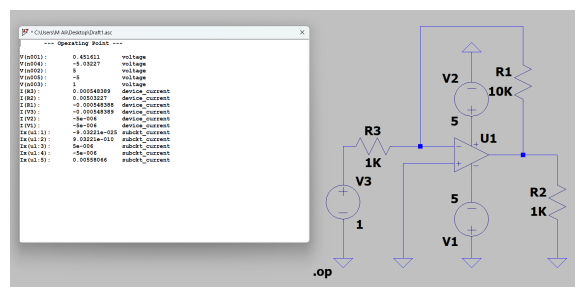



(b) LTspice

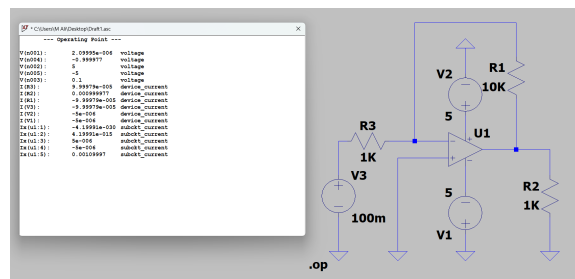


(b) LTspice



(b) LTspice

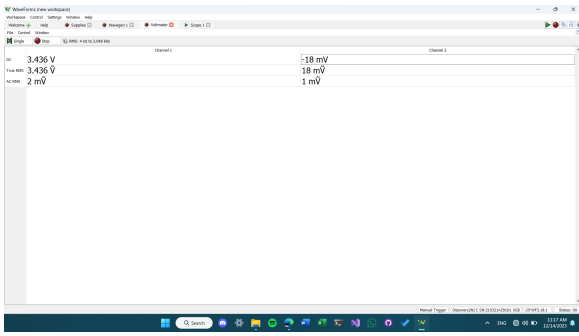


(a) Oscilloscope

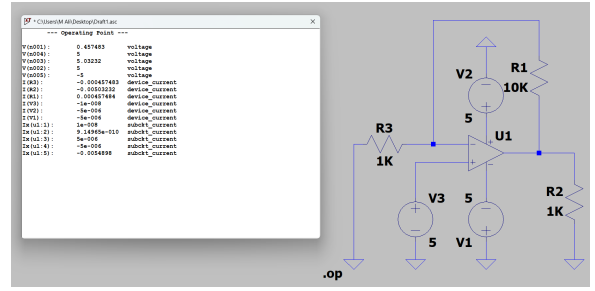


(b) LTSpice

Figure 4: Non-Inverting Op-Amp at 5 Volt

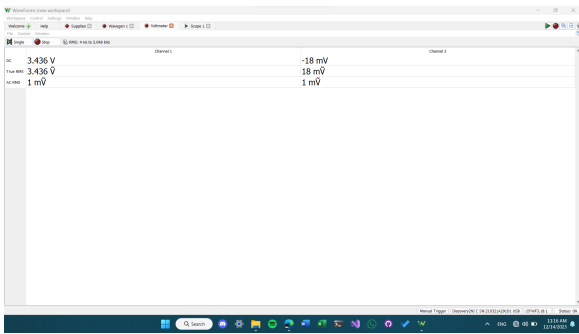


(a) Oscilloscope

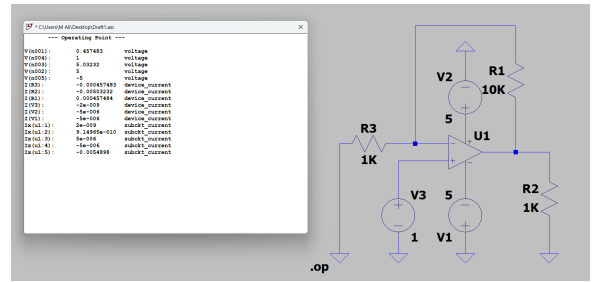


(b) LTSpice

Figure 5: Non-Inverting Op-Amp at 1 Volt

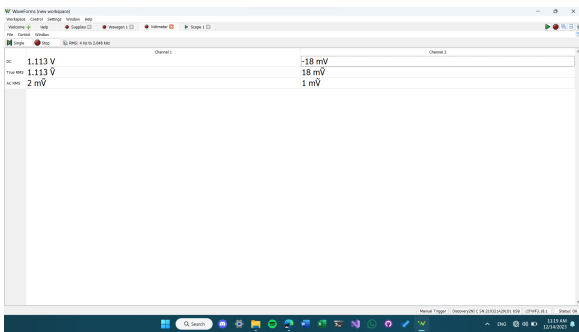

(a) Oscilloscope

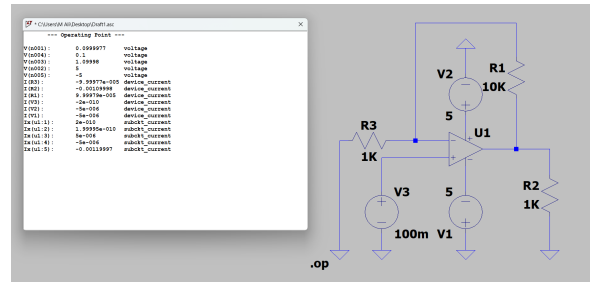

(b) LTSpice

Figure 6: Non-Inverting Op-Amp at 100 milliVolt